

Phil-Mont Mobile Radio Club

March 2023 Radio Labs

Adjustable Regulated Power Supply Kit





What we're going to do...

- ▶ Build a 1.25 to 25VDC Adjustable Regulated Power Supply
- ▶ Learn to identify electronic components
- ▶ Learn the Block Diagram of a Linear Power Supply
- ▶ Learn to recognize symbols on a Schematic Diagram
- ▶ Learn the function of each component in the Power Supply
- ▶ Learn basic assembly skills
- ▶ Learn basic soldering skills




Have FUN!!!

Electronic Components

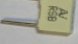

Step #1 - DIODES

D1	1N4007	
D2	1N4007	
D3	1N4007	
D4	1N4007	





Step #2 - RESISTORS

R1	10k ohm 1/4W 5%	Brown / Black / Orange / Gold	
R2	120 ohm 1/4W 5%	Brown / Red / Brown / Gold	
R3	1k ohm 1/4W 5%	Brown / Black / Red / Gold	


Step #3 - SMALL CAPACITORS

C4	0.15uF	
C5	10uF / 50V	


Step #4 - TERMINAL BLOCKS

18VAC INPUT	IN -/+ / IN -/+		
VDC OUTPUT	PWR / GND		

Step #5 - VARIABLE RESISTOR

VR1	4.7k ohm	
-----	----------	--


Step #6 - LED (LIGHT-EMITTING DIODE) INDICATOR

L1	"Red Drop"	
----	------------	---


Step #7 - LARGE CAPACITOR

C1	3300uF / 35V	
----	--------------	--


Step #8 - REGULATOR

U1	LM317	
----	-------	---

Linear Power Supply Block Diagram

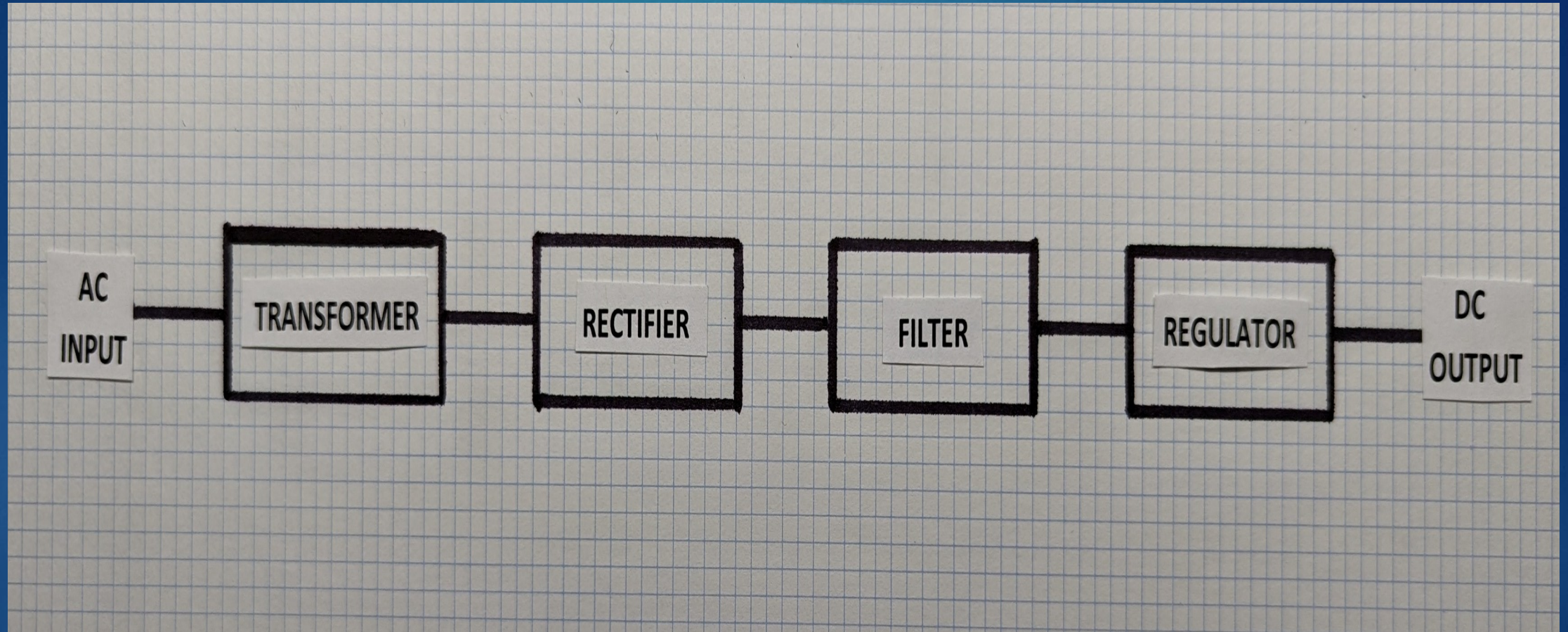


Transformer

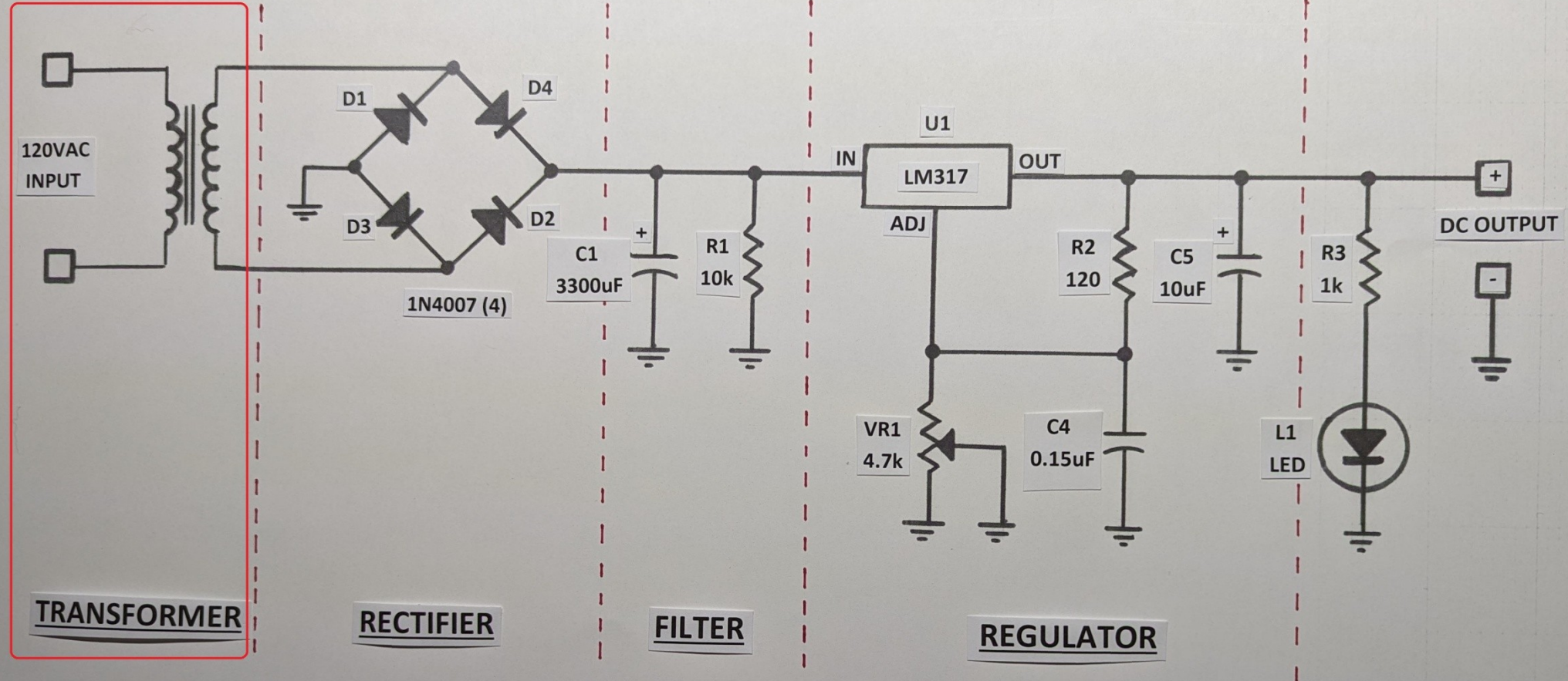


Transformer

- ▶ Transfer electrical energy from one circuit (Primary) to another (Secondary)
- ▶ Amount of energy transferred is proportional to the turns ratio (Primary to Secondary)


120 VAC Input Waveform

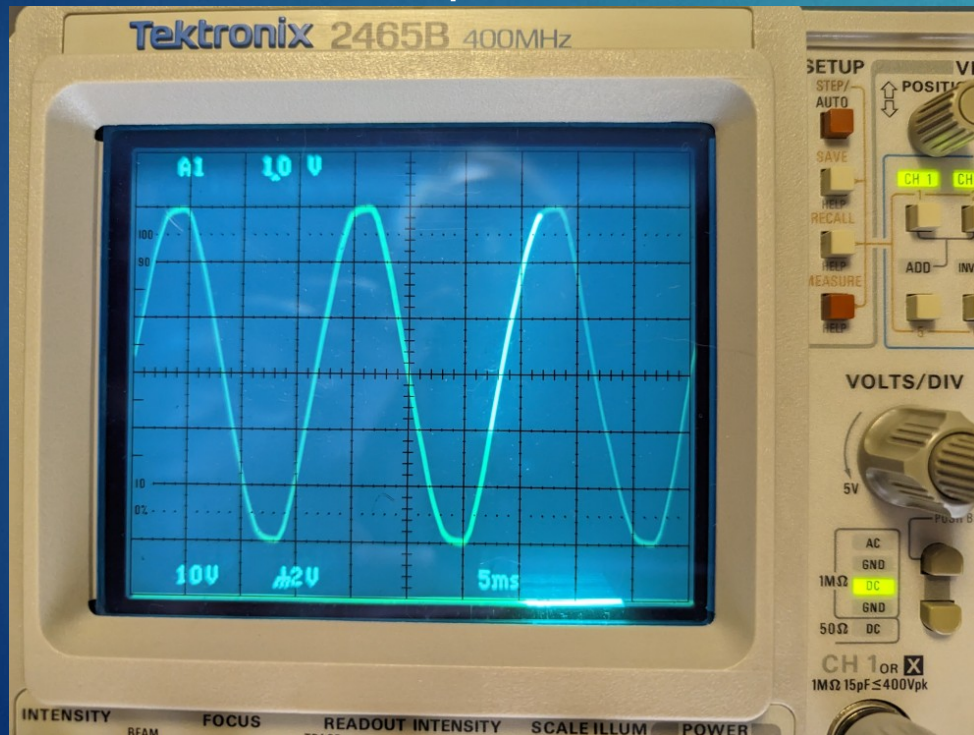

18VAC Output Waveform

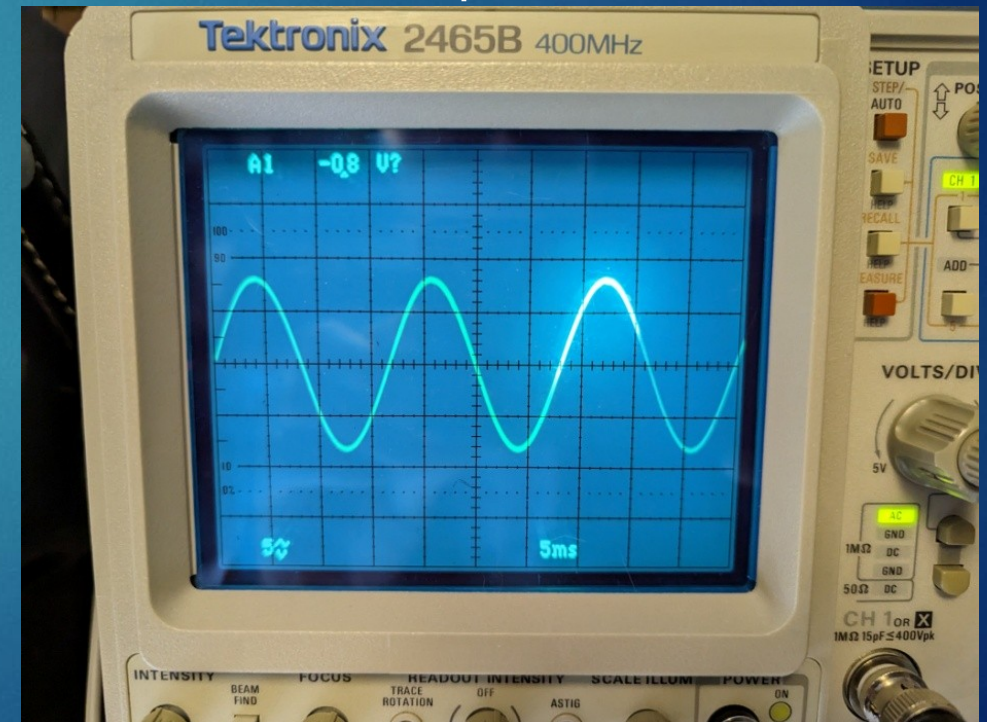


Rectifier

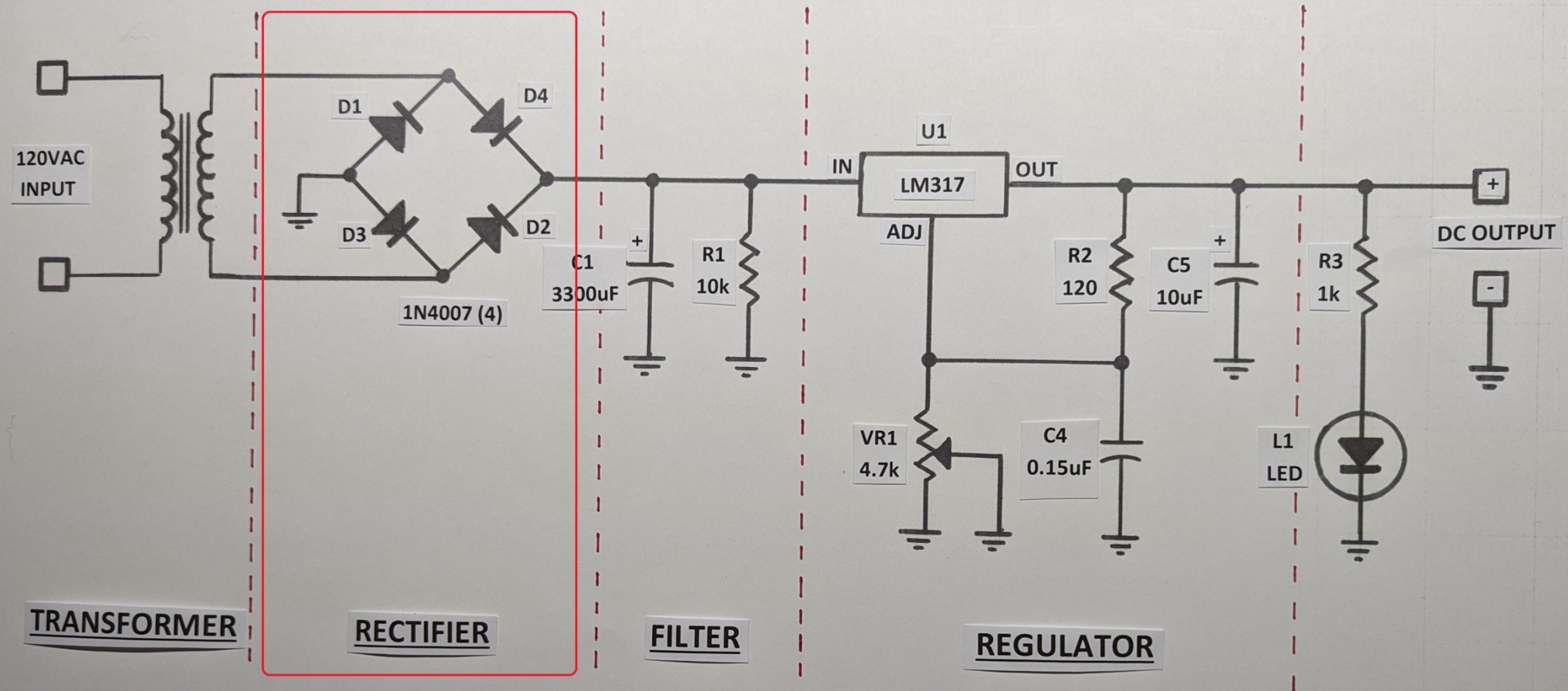


Rectifier

- ▶ A “Rectifier” is one use for a diode
- ▶ A diode allows current to flow in ONE direction
 - ▶ From Anode (Positive) to Cathode (Negative)
- ▶ Converts AC voltage to pulsating DC voltage


18VAC Input Waveform

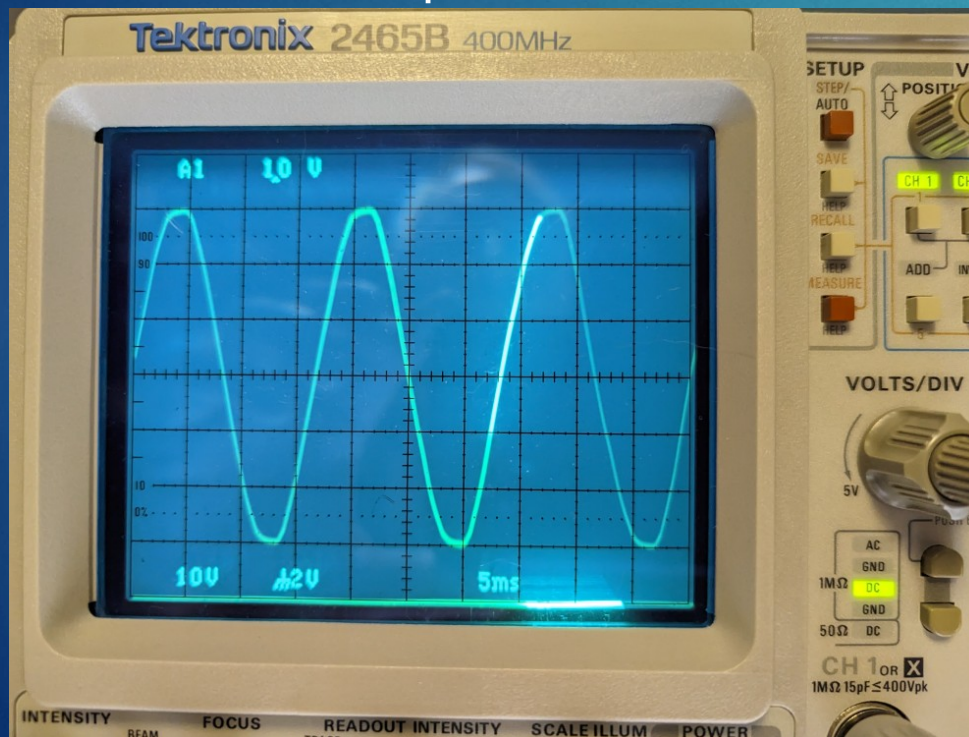

Pulsating DC Output Waveform

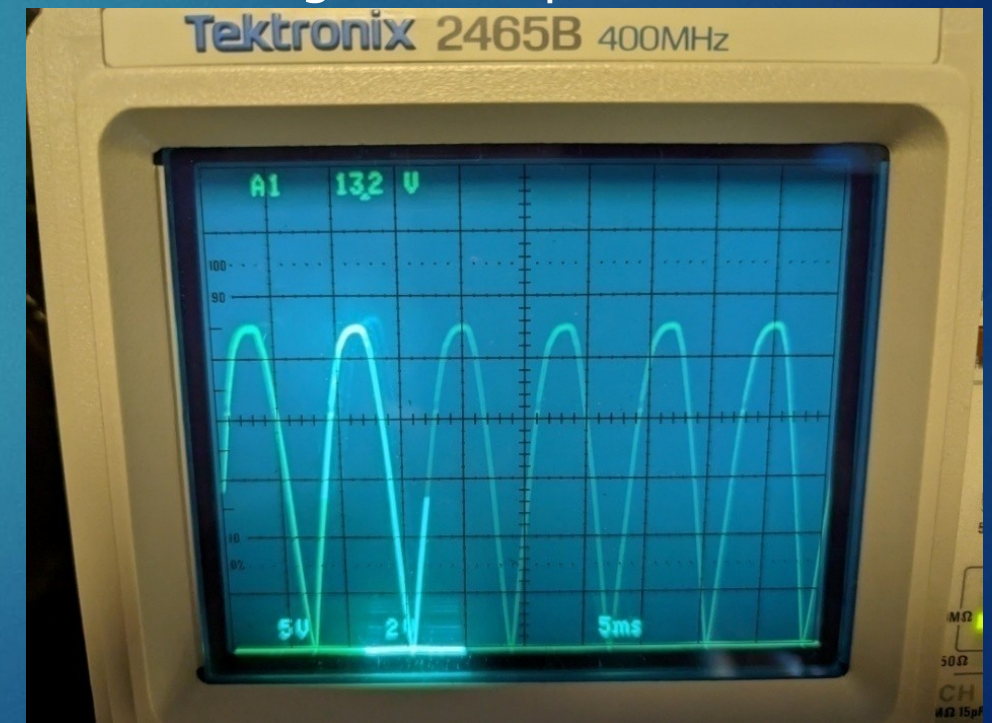


Filter

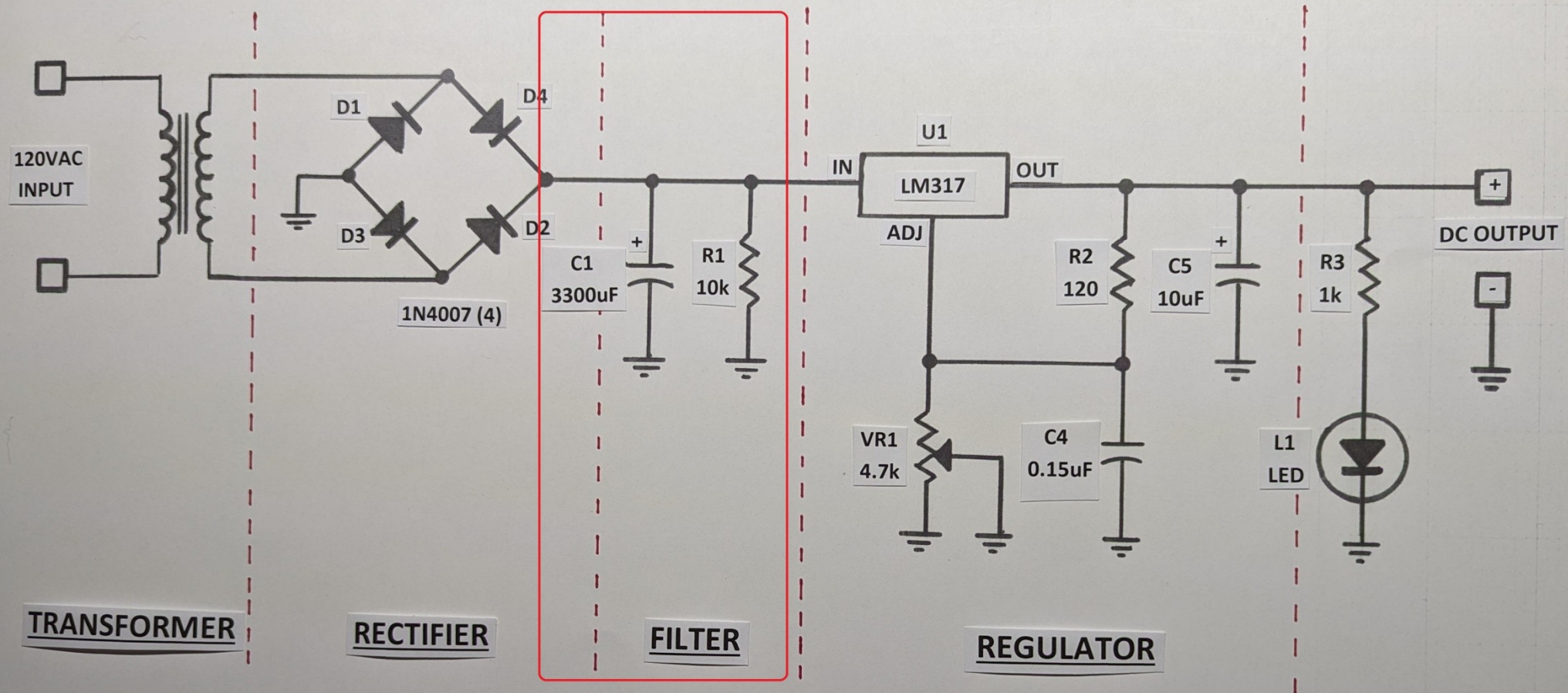


Filter

- ▶ A “Filter” is one use for a capacitor
- ▶ Stores electrical energy between parallel plates
- ▶ Electrolytic Capacitors are polarity-sensitive
- ▶ “Smooths” the applied pulsating DC voltage
- ▶ Capacitance here is $2\mu\text{F}$

Pulsating DC Input Waveform

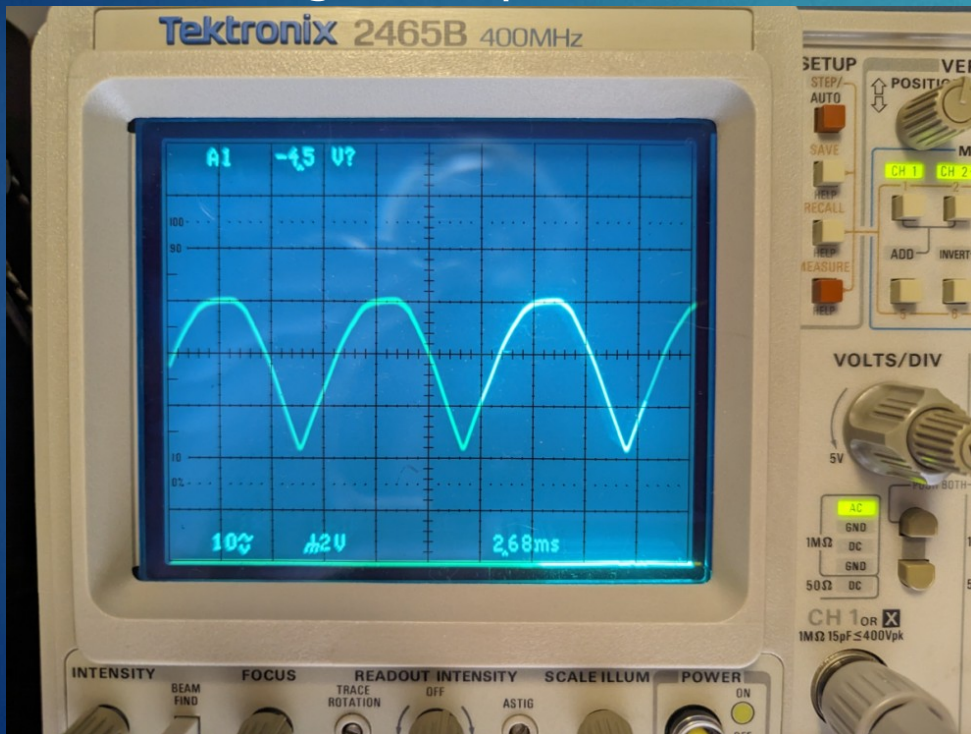

DC Output Waveform w/Ripple

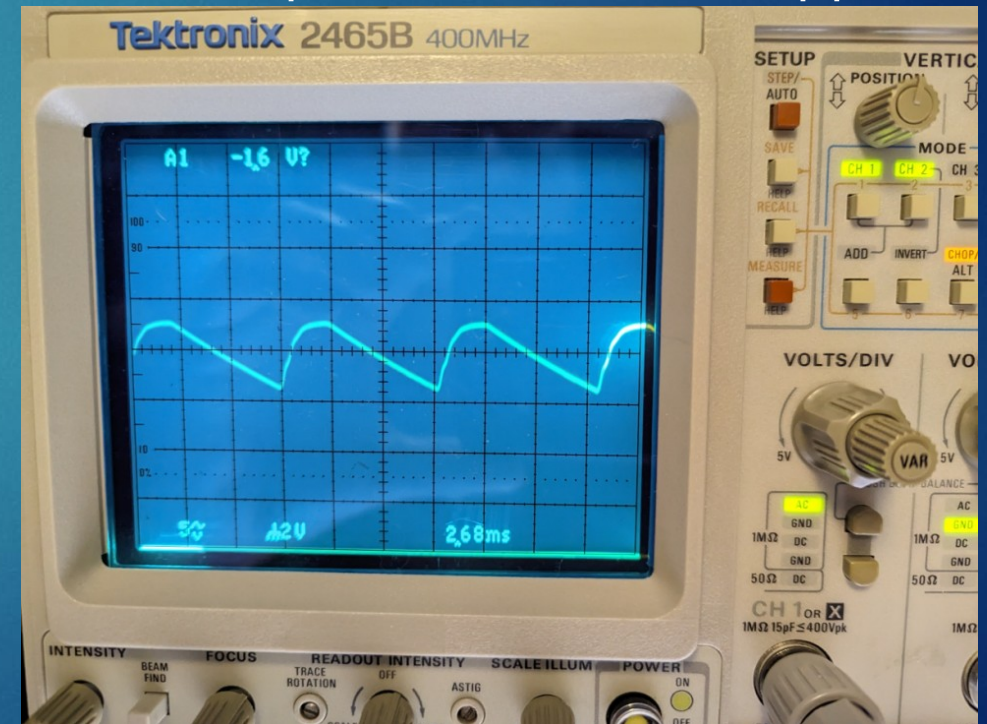

100




100

The image shows a Tektronix 2465 oscilloscope with a digital display. The screen displays a periodic waveform with a peak-to-peak voltage of 1.6 V and a period of 2.68 ms. The waveform is a red trace on a blue grid. The top of the screen shows 'A1 -1.6 V?' and the bottom shows '2.68ms'. The right side of the image shows the physical controls of the oscilloscope, including the 'SETUP' section with 'STEP/AUTO', 'SAVE', 'RECALL', 'MEASURE', and 'HELP' buttons, and the 'VERTICAL' section with 'POSITION', 'MODE', 'CH 1', 'CH 2', 'CH 3', 'ADD', 'INVERT', 'CHOP', and 'ALT' buttons. Below these are 'VOLTS/DIV' and 'VARIABLE' knobs, and a 'CH 1 OR 2' selector.



Regulator

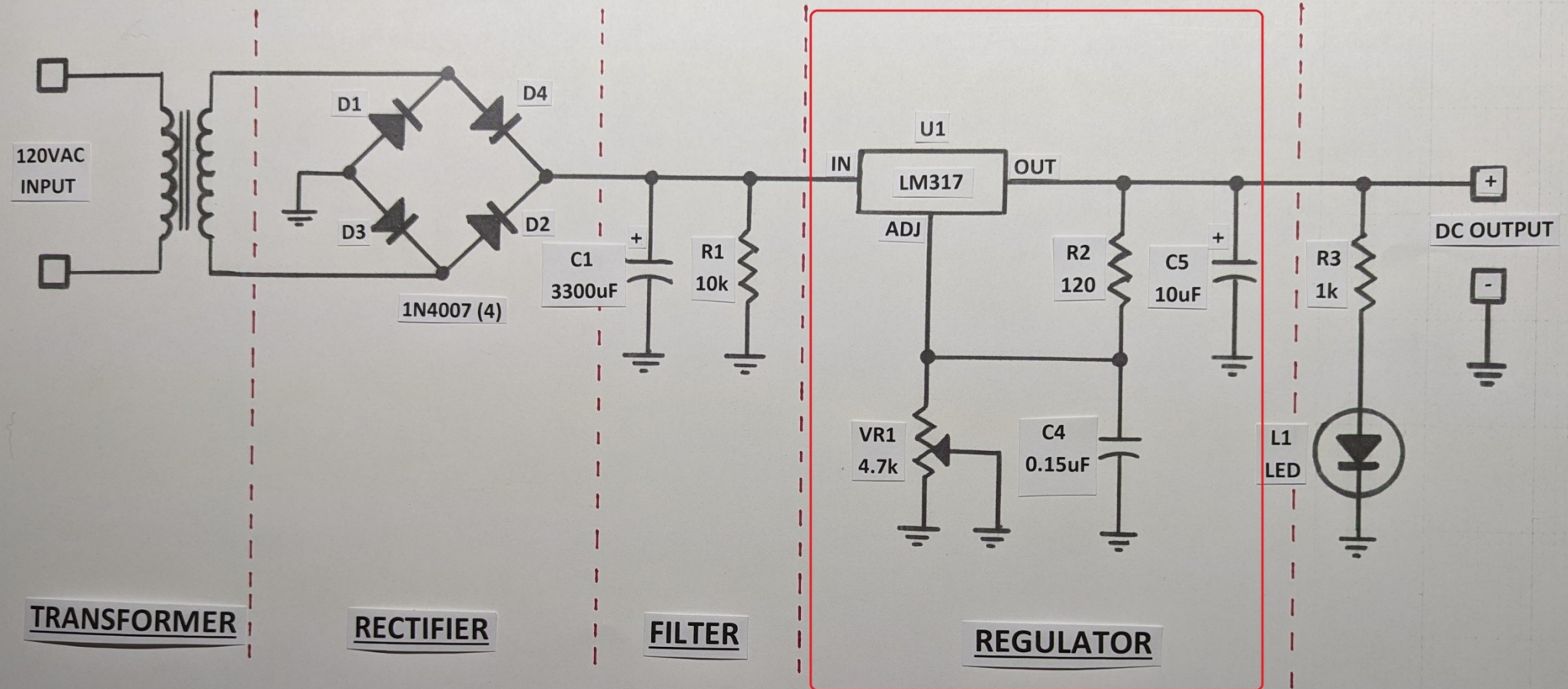


Regulator


- ▶ Generates a constant output voltage from an unstable (varying) input voltage
- ▶ Three-Terminal Adjustable Regulator Integrated Circuit (IC) type LM317
- ▶ CAUTION!!! The IC get HOTTER as the current being drawn increases
- ▶ Different Regulator ICs for Positive and Negative Output Voltages
 - ▶ Fixed Positive Regulators: 7805 / 7812 / 7815 / 7824 / others
 - ▶ Fixed Negative Regulators: 7905 / 7912 / 7915 / others
 - ▶ Adjustable Negative Regulators: 337

CAUTION: Terminals are NOT the same for different devices!


Assembled Power Supply

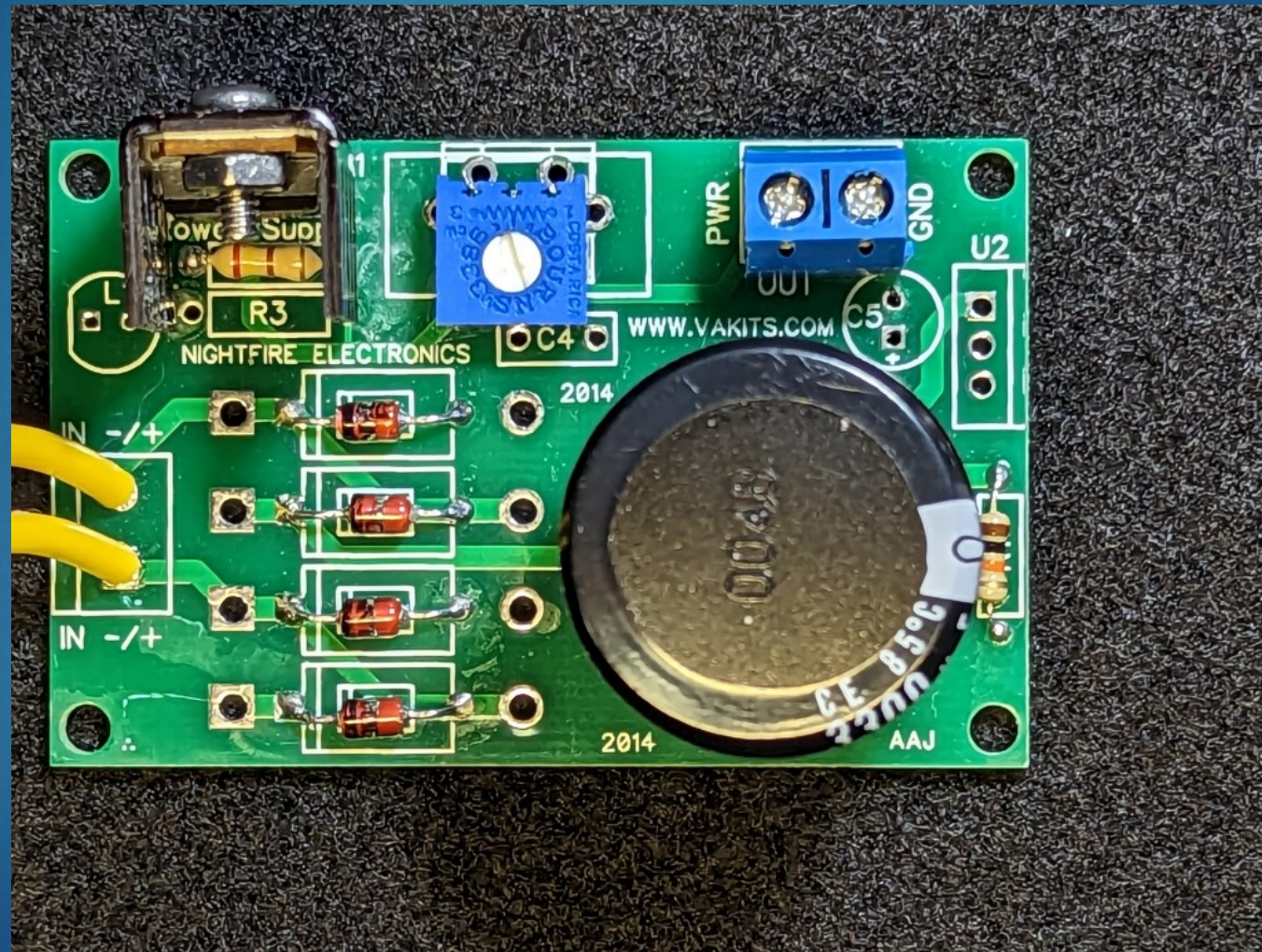

Printed Circuit Board

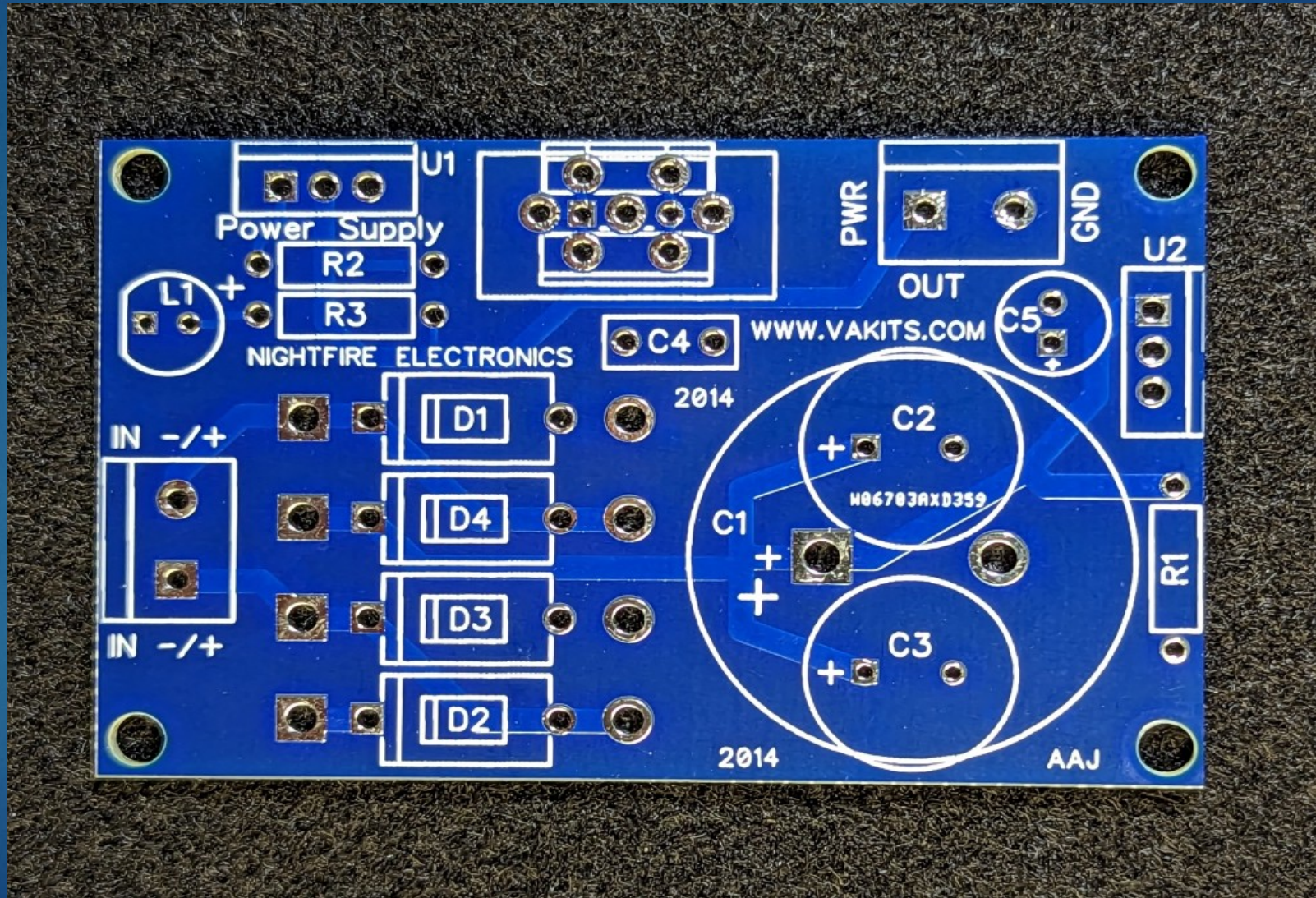


Assembly Drawing

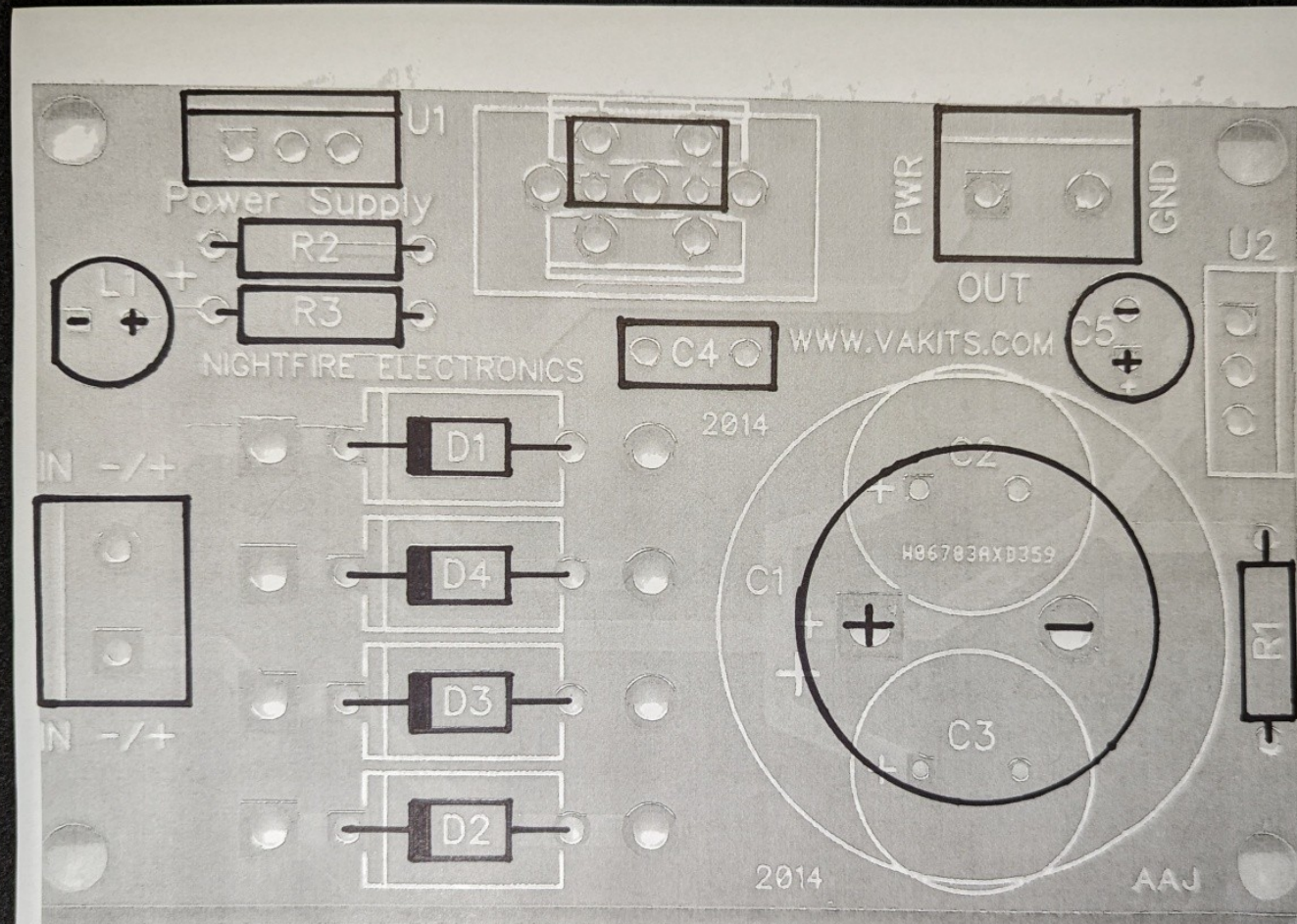


Component Installation - Step 1

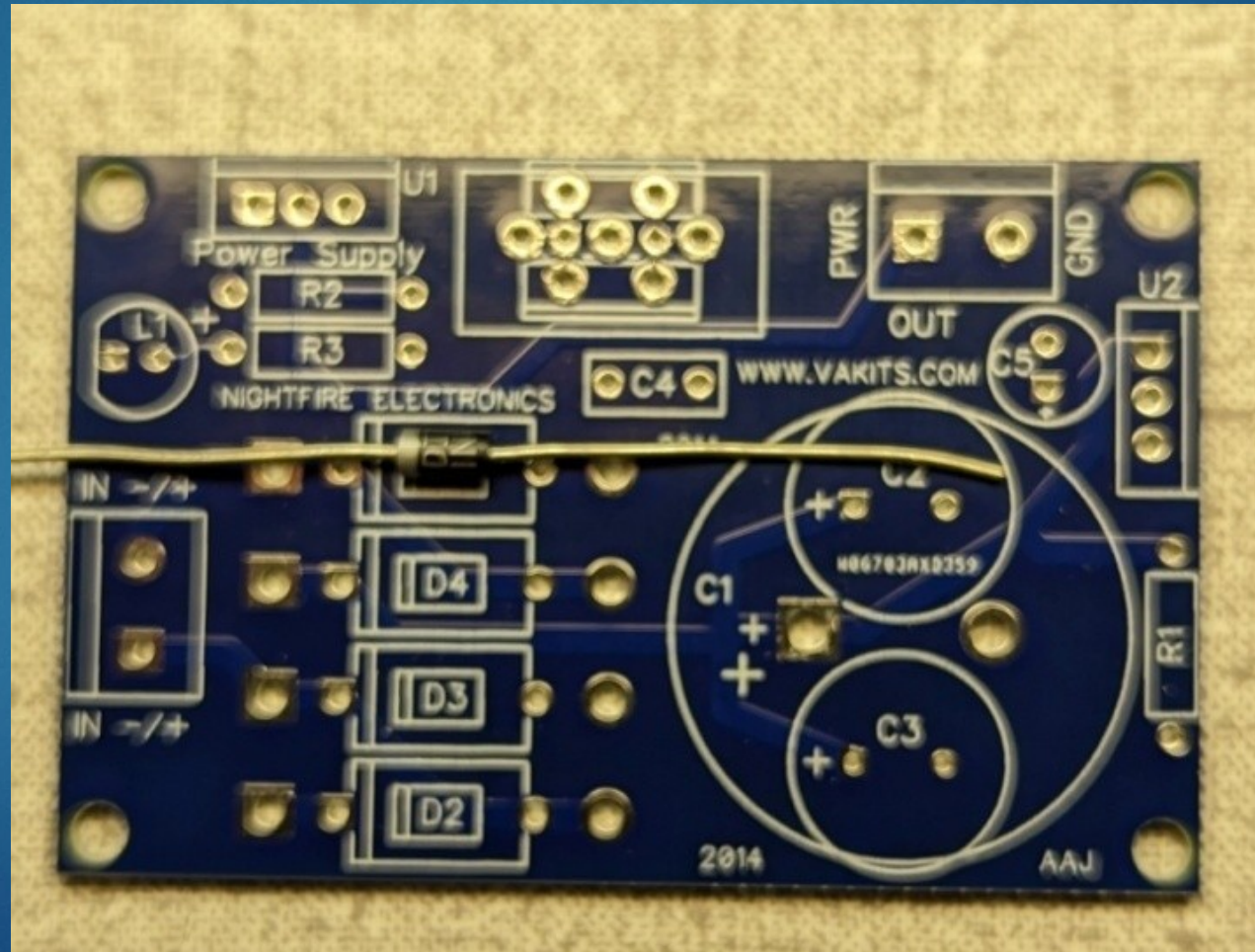- Step 1 - Place component over installation location




Component Installation - Step 2

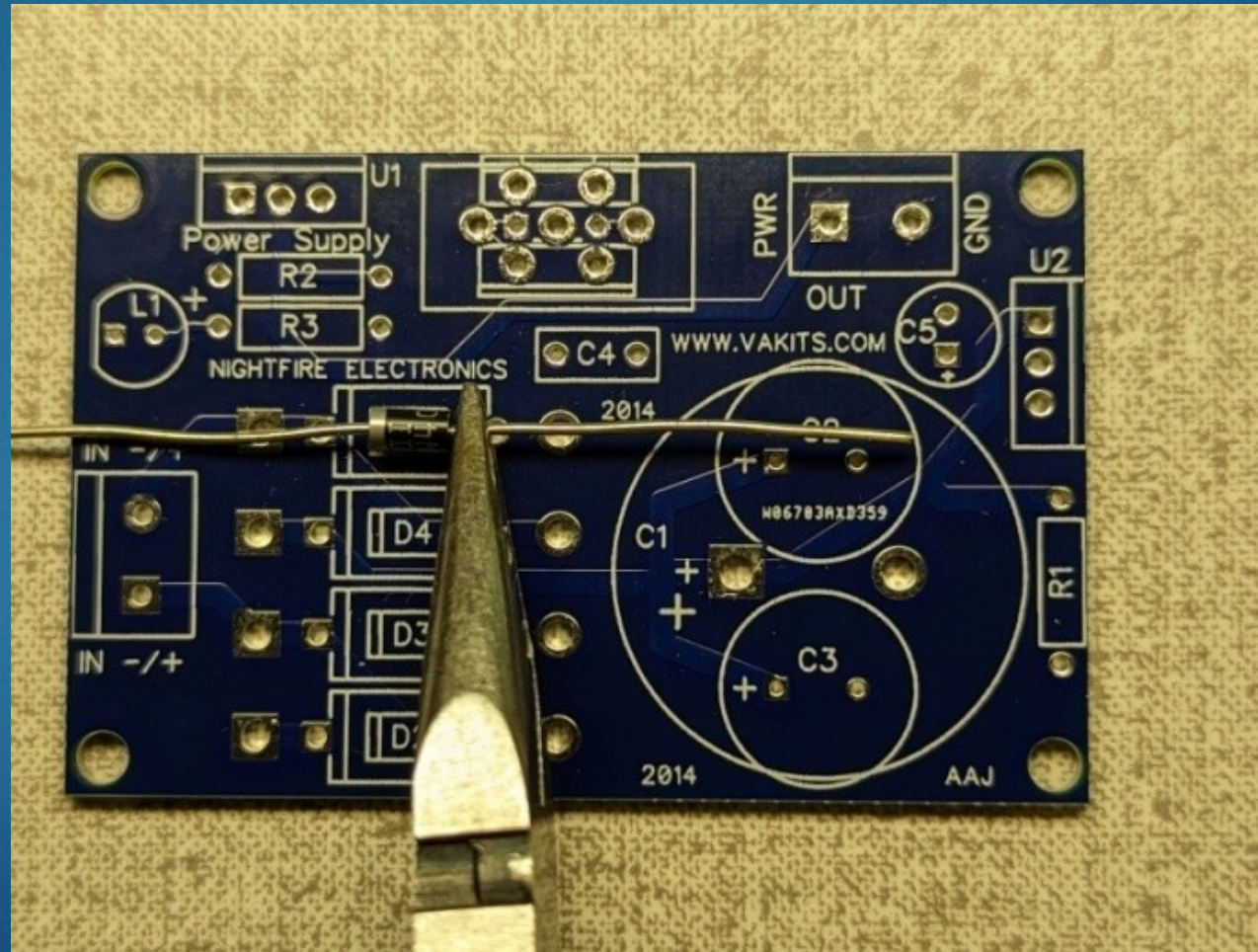- Step 2 – Grab component lead with pliers against body




Component Installation - Step 3

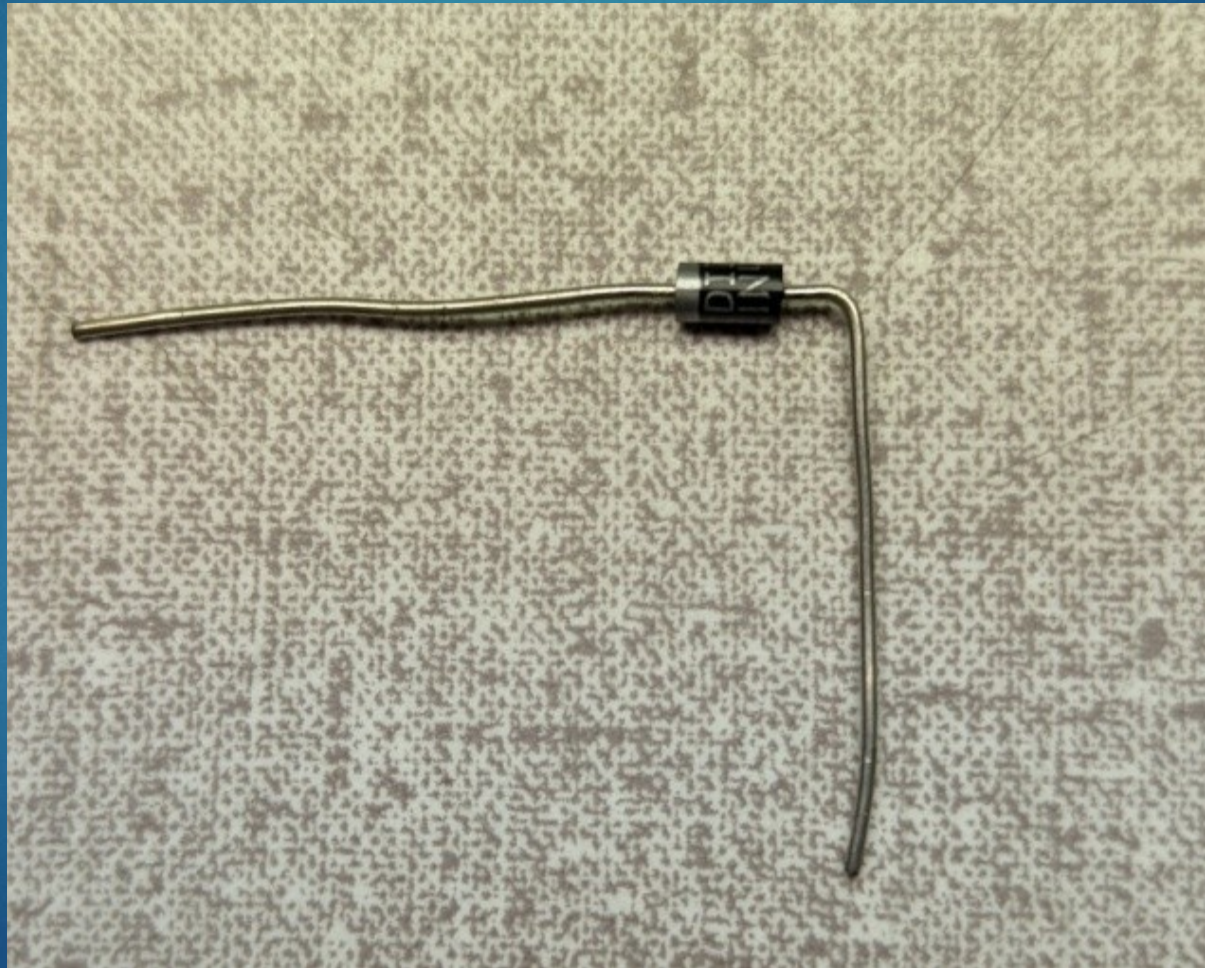- ▶ Step 3- Lift component and bend lead as shown




Component Installation - Step 4

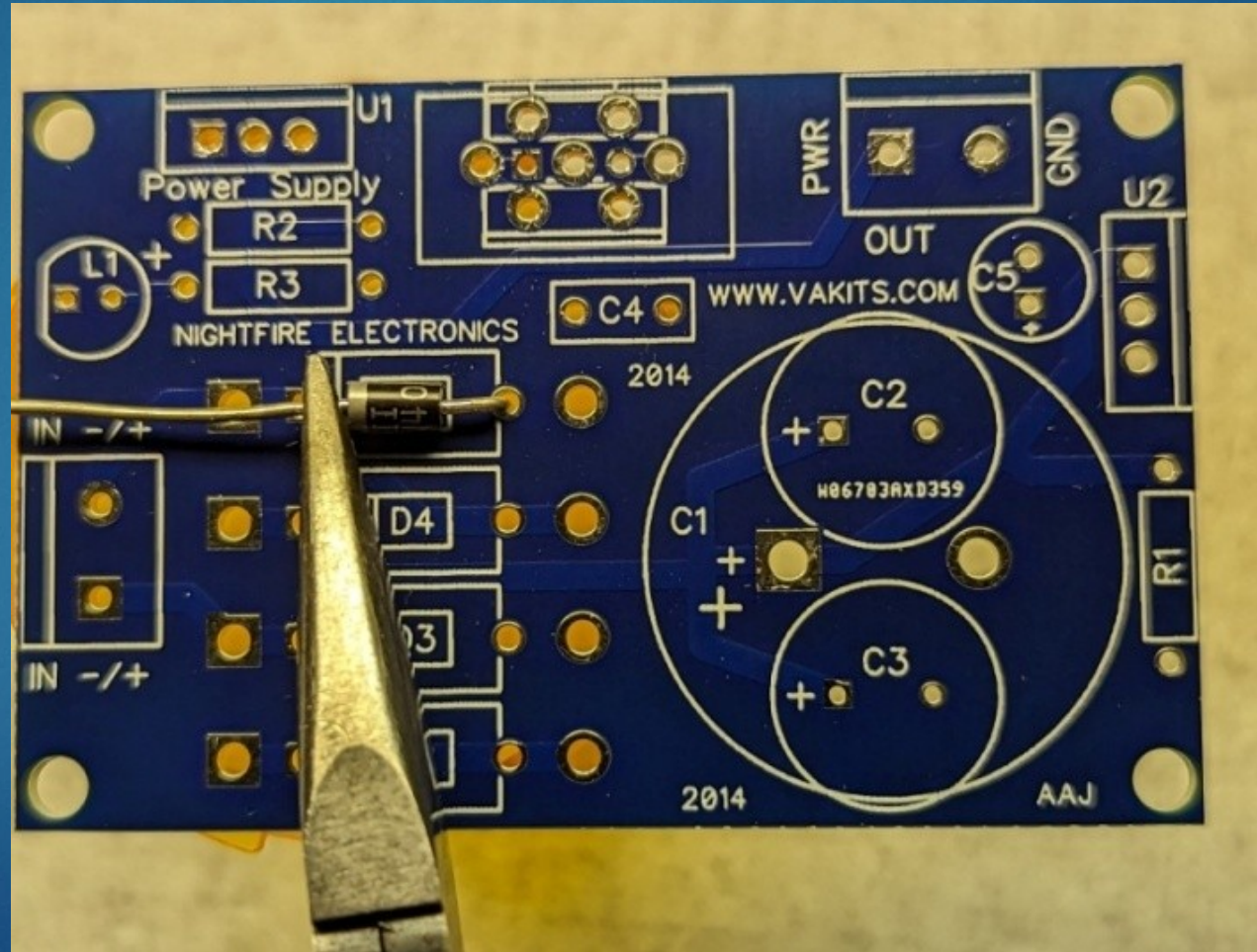- ▶ Step 4 – Insert bent lead and grab the other lead as shown




Component Installation - Step 5

- ▶ Step 5 – Bend second lead as shown

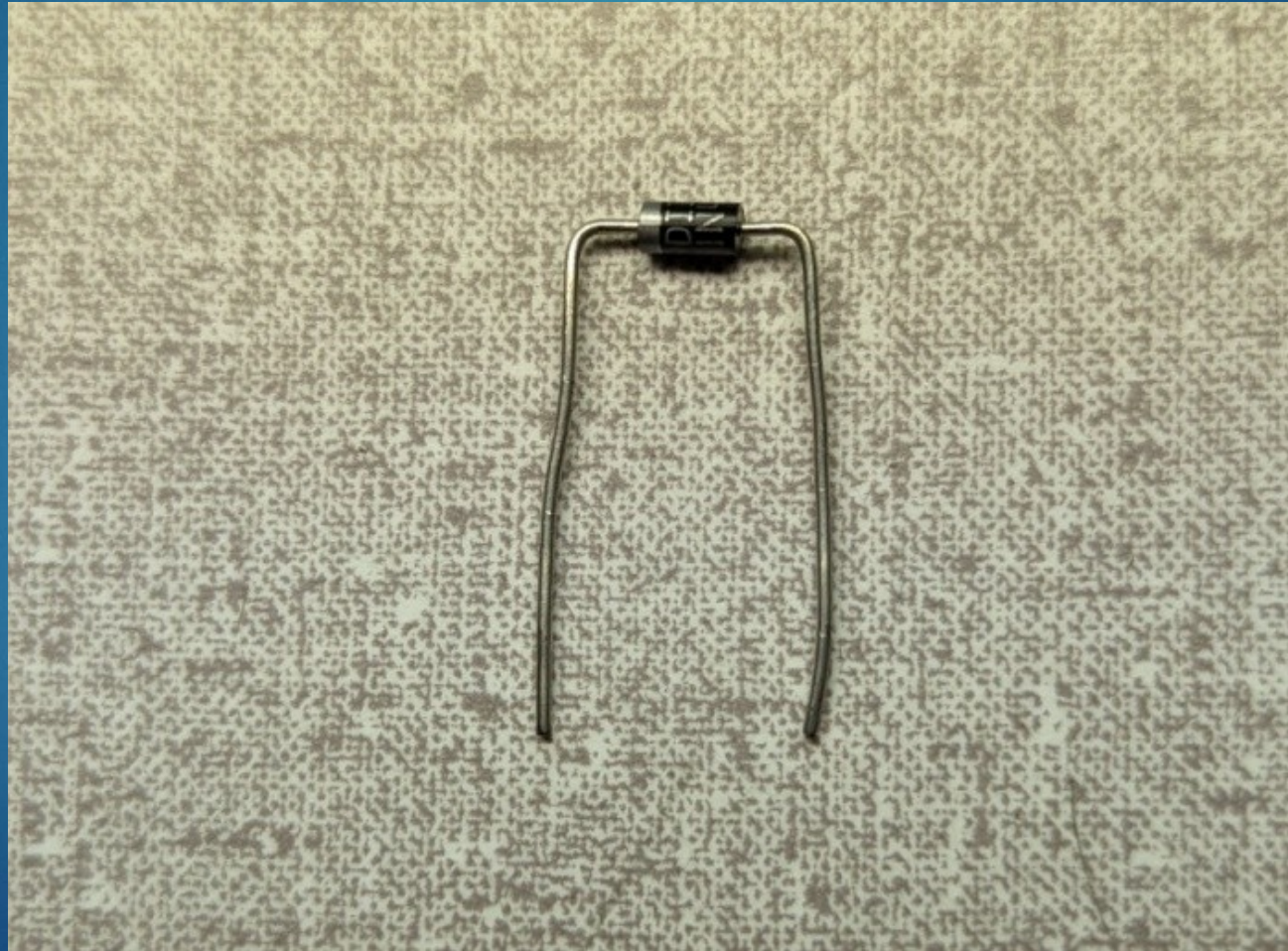


Component Installation - Step 6

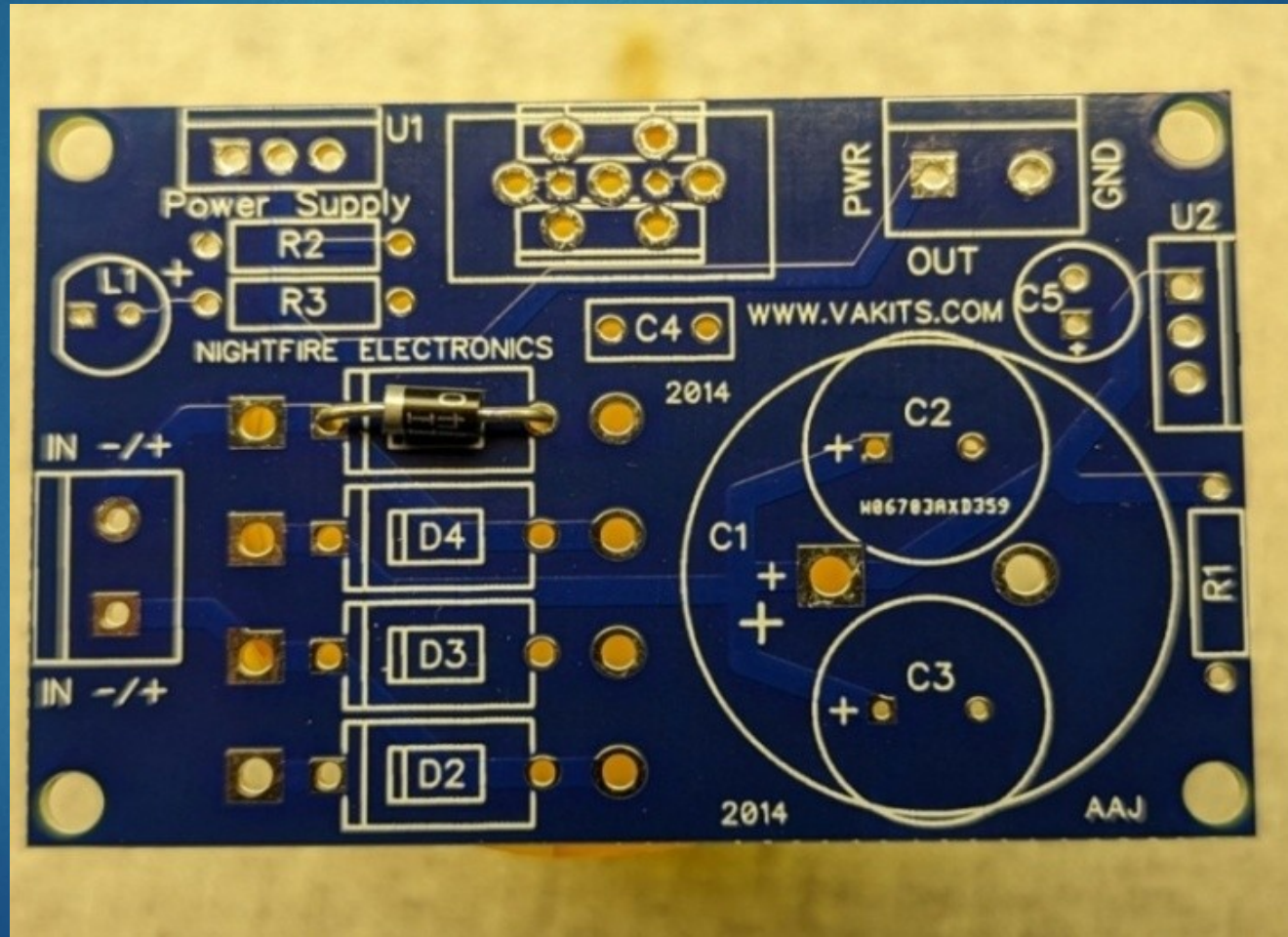- Step 6 – Insert component into position




Component Installation - Step 7

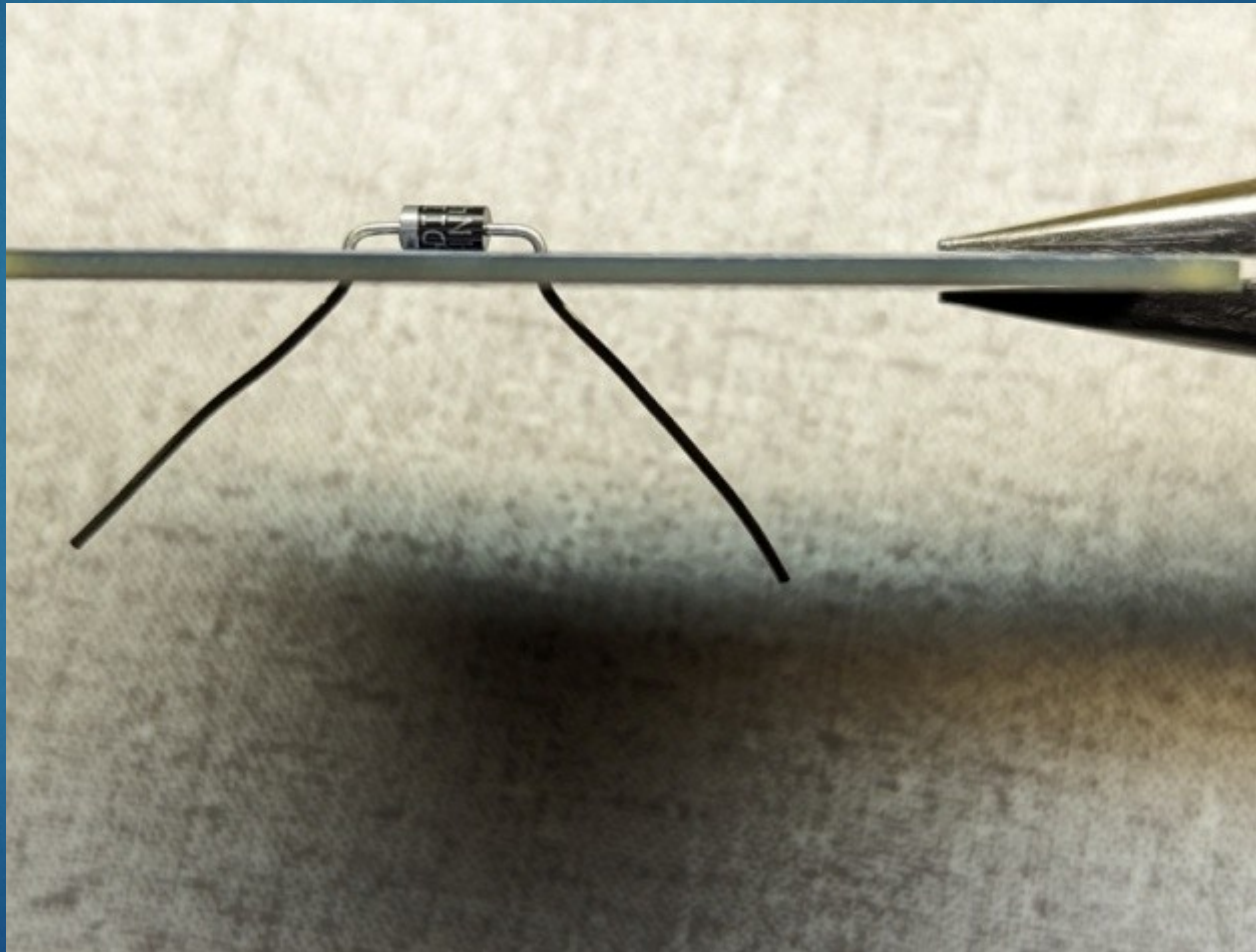- ▶ Step 7 - Bend leads as shown to hold component in place




Soldering - Step 1

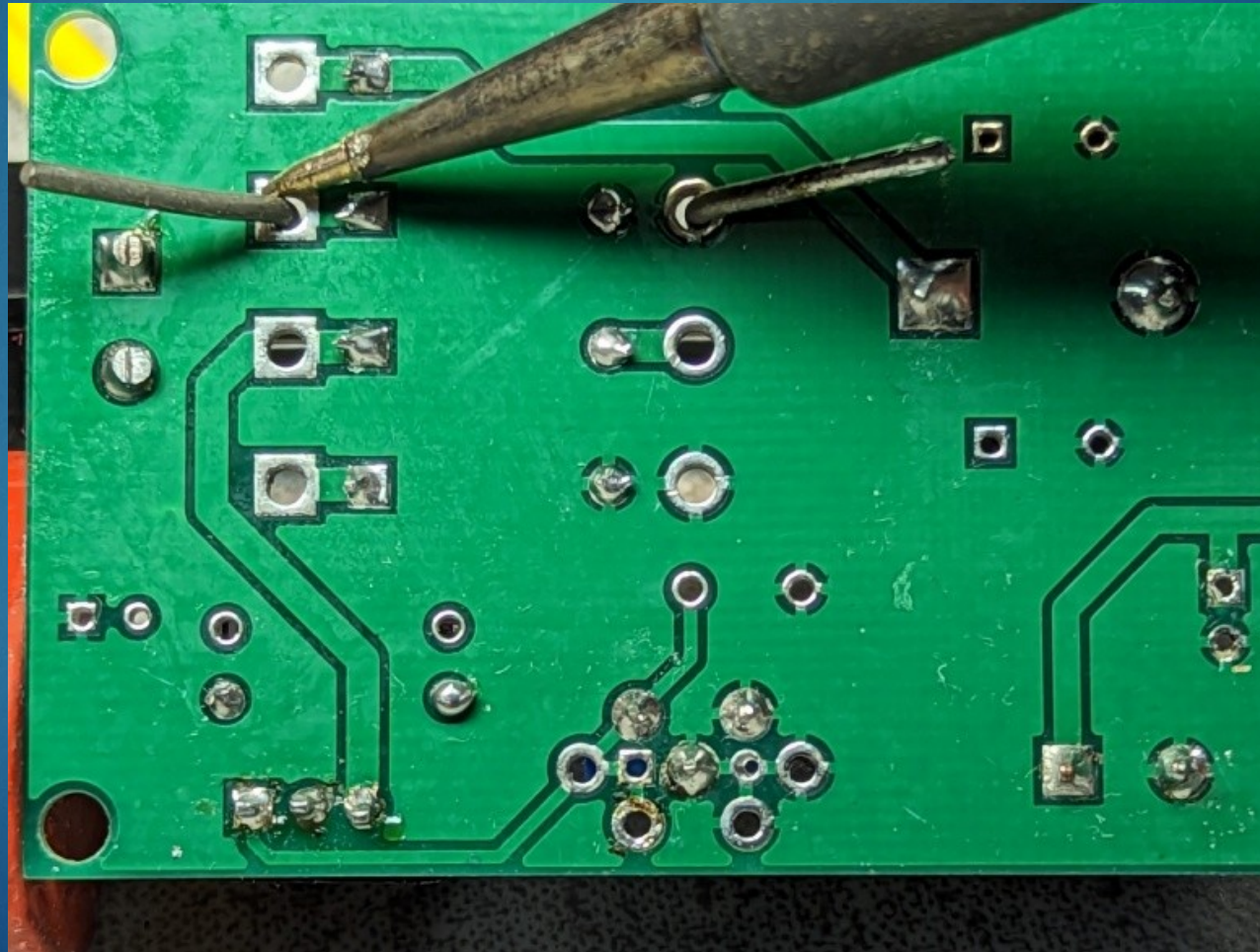- ▶ Step 1 – Place Iron against BOTH board AND component lead to heat




Soldering - Step 2

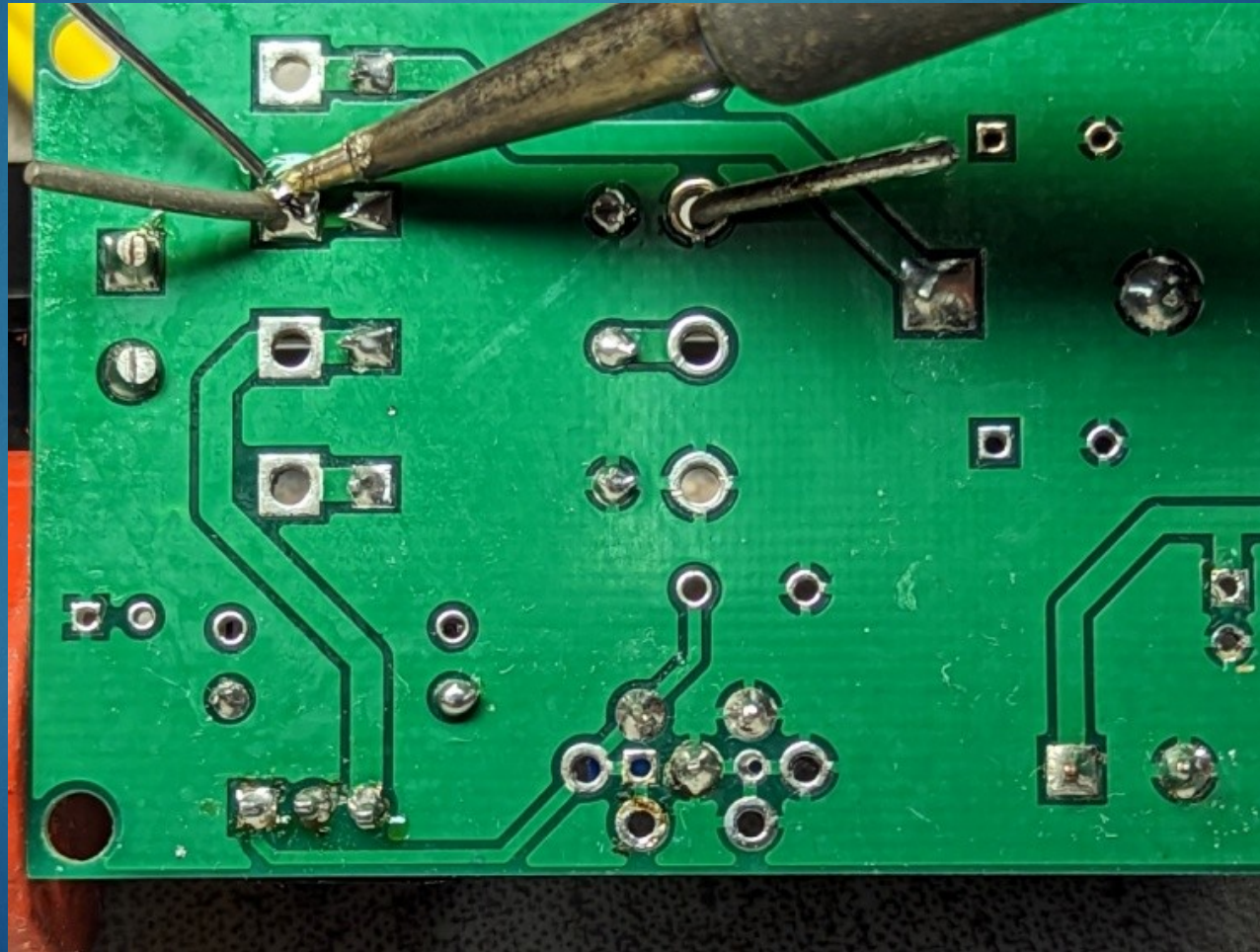- ▶ Step 2 – After 10-15 seconds GENTLY push solder against Iron Tip, component lead, and board until solder starts melting



Soldering - Step 3

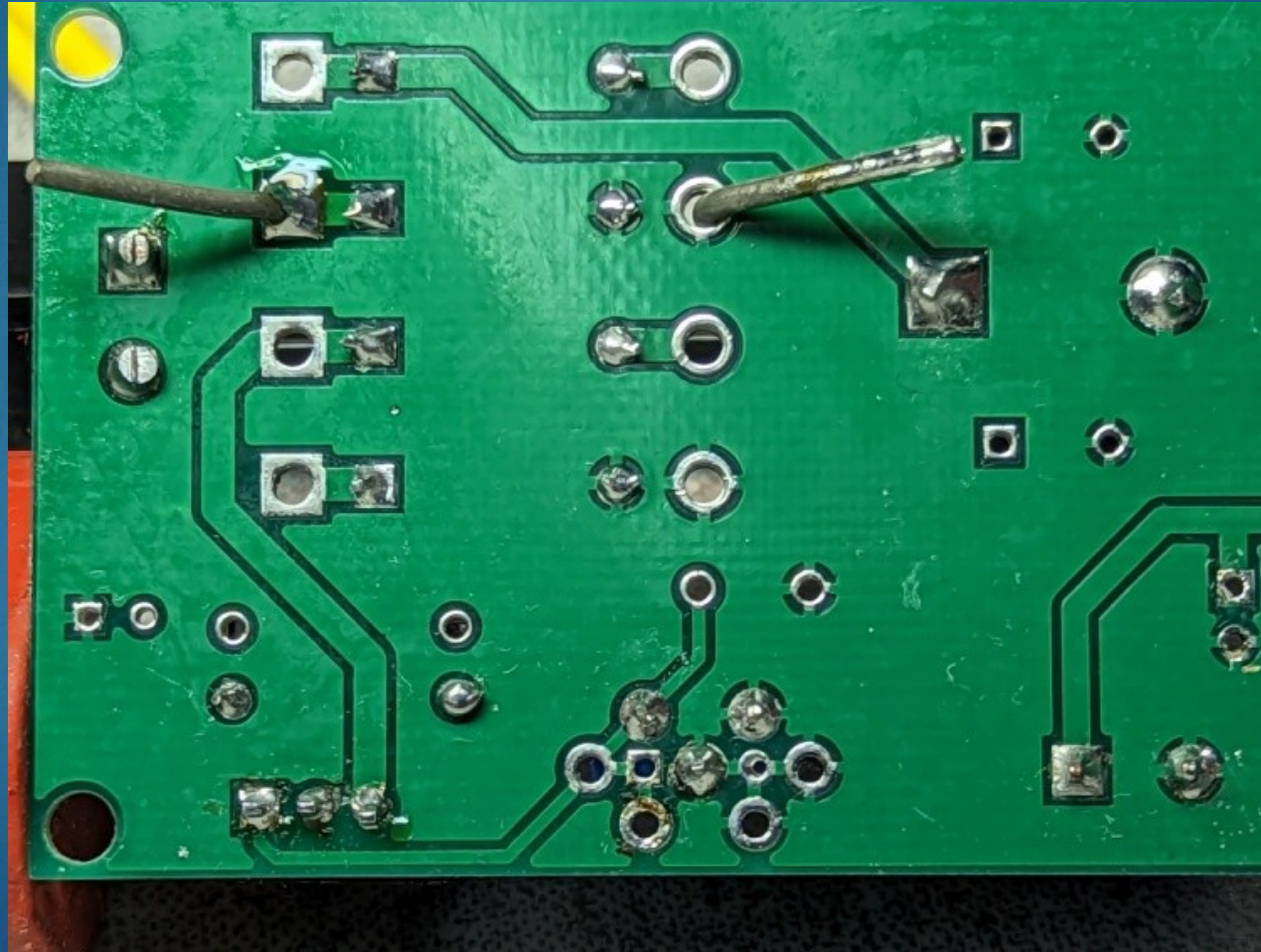- ▶ Step 3 – When a small mound of solder forms, remove solder and then the Iron, KEEPING THE JOINT STILL for a few seconds for solder to set



Assembly (1 of 3)

- ▶ DIODES - Observe Polarity! Band identifies Cathode (Negative) Lead

- ▶ D1 1N4007

- ▶ D2 1N4007

- ▶ D3 1N4007

- ▶ D4 1N4007

- ▶ RESISTORS

- ▶ R1 10k 1/4W 5% Brown - Black - Orange - Gold

- ▶ R2 120 1/4W 5% Brown - Red - Brown - Gold

- ▶ R3 1k 1/4W 5% Brown - Black - Red - Gold

Assembly (2 of 3)

- ▶ SMALL CAPACITORS
 - ▶ C4 0.15uF
 - ▶ C5 10uF / 50V Observe Polarity! Negative Lead is marked

- ▶ TERMINAL BLOCKS
 - ▶ 18VAC Input IN -/+ / IN -/+
 - ▶ VDC Output PWR / GND

- ▶ VARIABLE RESISTOR
 - ▶ VR1 4.7k ohms

Assembly (3 of 3)

- ▶ LED (LIGHT-EMITTING DIODE) INDICATOR
 - ▶ L1 “Red Drop” Observe Polarity! Positive Lead is longer

- ▶ LARGE CAPACITOR
 - ▶ C1 3300uF / 35V Observe Polarity! Negative Lead is marked

- ▶ VOLTAGE REGULATOR
 - ▶ U1 LM317 FLAT SIDE faces OUTWARD on PCB

Pre-Test Inspection / Prep

- ▶ Visual Inspection
 - ▶ Diode Banded-End pointing toward Input Terminal Block
 - ▶ Large Capacitor NEGATIVE pointing toward 10k resistor
 - ▶ Small capacitor NEGATIVE pointing toward Output Terminal Block
 - ▶ Ensure all component leads have been trimmed on bottom
 - ▶ Ensure all joints have been soldered
- ▶ Check for Solder Bridges (Shorts)
- ▶ Set VR1 to Mid-Rotation

Smoke Test!

- ▶ Connect Power Transformer to AC Input Terminal Block
- ▶ Set DMM to read DC VOLTS
- ▶ Connect DMM to Output Terminal Block
- ▶ GO! Plug the Transformer into a Wall Outlet
- ▶ LED should illuminate - if it doesn't, UNPLUG IMMEDIATELY!!!
- ▶ DMM should read approximately 12 VDC
- ▶ IT WORKS!!!

Functional Test

- ▶ Using a small screwdriver, turn the Variable Resistor fully counterclockwise
- ▶ DMM should read approximately 1.25 VDC
- ▶ Using a small screwdriver, turn the Variable Resistor fully clockwise
- ▶ DMM should read approximately 25 VDC
- ▶ Using a small screwdriver, adjust the Variable Resistor until the DMM reads 12.6 VDC
- ▶ CONGRATULATIONS! COMPLETE SUCCESS!!!

In Case of Difficulty

- ▶ Go back to Pre-Test Inspection / Prep
- ▶ Voltage Checks
 - ▶ Voltage across Input Terminal Block should be approximately 20.8 VAC
 - ▶ Voltage across R1 should be approximately 27.5 VDC